

Lecture 2: Computer Abstractions & Technology

- Last Time
 - Course Overview
 - Introduction to Computer Architecture
- Today
 - Announcements, HW Late Policy
 - Review of last lecture
 - Computer elements
 - Transistors, wires, pins
 - Introduction to performance
 - Handout HW #1

Recap of Lecture 1

How to design something:


- List goals
- List constraints
- Generate ideas for possible designs
- Evaluate the different designs
- Pick the best design
- Refine it

In reality, this process is iterative.

As constraints change, best design will change too.

[Use kitchen remodel as example of design process]

Intel 4004 - 1971

 

- The first microprocessor
- 2,300 transistors
- 108 KHz
- 10 μ m process

Intel Pentium IV - 2001



- "State of the art"
 - Three years ago!
- 42 million transistors
- 2GHz
- 0.13 μ m process
- Could fit ~15,000 4004s on this chip!

UTCS

Lecture 2

5

Don't forget the simple view

All a computer does is

- Store and move data
- Communicate with the external world
- Do these two things conditionally
- According to a recipe specified by a programmer

It's complex because

- We want it to be fast
- We want it to be reliable and secure
- We want it to be simple to use
- It must obey the laws of physics

UTCS

Lecture 2


6

Lecture 2 - Computer Abstractions & Technology

Computer Elements

- **Transistors (computing)**
 - How can they be connected to do something useful?
 - How do we evaluate how fast a logic block is?
- **Wires (transporting)**
 - What and where are they?
 - How can they be modeled?
- **Memories (storing)**
 - SRAM vs. DRAM

What Comes out of the Fab?


 


UTCS

Lecture 2

9

The Mighty Transistor!

  

AMER

(a)


UTCS

Lecture 2



10

Transistor As a Switch

- Ideal Voltage Controlled Switch

 


  - Three terminals
 - Gate
 - Drain
 - Source




Abstractions in Logic Design

 - In physical world
 - Voltages, Currents
 - Electron flow
- In logical world - abstraction
 - $V < V_{lo} \Rightarrow$ "0" = FALSE
 - $V > V_{hi} \Rightarrow$ "1" = TRUE
 - In between - forbidden
- Simplify design problem



Basic Technology: CMOS

- **CMOS: Complementary Metal Oxide Semiconductor**
 - NMOS (N-Type Metal Oxide Semiconductor) transistors
 - PMOS (P-Type Metal Oxide Semiconductor) transistors
- **NMOS Transistor**
 - Apply a HIGH (V_{dd}) to its gate turns the transistor into a "conductor"
 - Apply a LOW (GND) to its gate shuts off the conduction path
- **PMOS Transistor**
 - Apply a HIGH (V_{dd}) to its gate shuts off the conduction path
 - Apply a LOW (GND) to its gate turns the transistor into a "conductor"

 



UTCS

Slide courtesy of D. Patterson




Lecture 2

13

Basic Components: CMOS Inverter

  

• **Inverter Operation**

   

UTCS


Slide courtesy of D. Patterson

Lecture 2

14

What can you build with transistors?

 - Logic Gates
 - Inverters, AND, OR, arbitrary



- Buffers (drive large capacitances, long wires, etc.)
- Memory elements
 - Latches, registers, SRAM, DRAM



UTCS

Lecture 2

15

Basic Components: CMOS Logic Gates



NAND Gate

  

UTCS

Slide courtesy of D. Patterson



NOR Gate

  

Lecture 2

16

Gate Comparison

  

- If PMOS transistors is faster:
 - It is OK to have PMOS transistors in series
 - NOR gate is preferred
 - NOR gate is preferred also if $H \rightarrow L$ is more critical than $L \rightarrow H$
- If NMOS transistors is faster:
 - It is OK to have NMOS transistors in series
 - NAND gate is preferred
 - NAND gate is preferred also if $L \rightarrow H$ is more critical than $H \rightarrow L$

UTCS

Slide courtesy of D. Patterson

Lecture 2

17

The Ugly Truth

- Transistors are not ideal switches!
 - Gate Capacitance (C_g)
 - Source-to-Drain resistance (R)
 - Drain capacitance
- Issues
 - Delay - actually takes real time to turn transistors on and off
 - Power/Energy
 - Noise (from transistors, power rails)
- But - we can change transistor size
 - Increase C_g , but decrease R


UTCS

Lecture 2

18

Ideal (CS) versus Reality (EE)

 - When input 0 → 1, output 1 → 0 but NOT instantly
 - Output goes 1 → 0: output voltage goes from V_{dd} (2.5v) to 0v
- When input 1 → 0, output 0 → 1 but NOT instantly
 - Output goes 0 → 1: output voltage goes from 0v to V_{dd} (2.5v)
- Voltage does not like to change instantaneously




UTCS

Slide courtesy of D. Patterson

Lecture 2

19

Fluid Timing Model

 

- Water ↔ Electrical Charge Tank Capacity ↔ Capacitance (C)
- Water Level ↔ Voltage Water Flow ↔ Charge Flowing (Current)
- Size of Pipes ↔ Strength of Transistors (G)
- Time to fill up the tank ~ C / G Resistance R = 1/G


UTCS

Slide courtesy of D. Patterson

Lecture 2

20

Series Connection

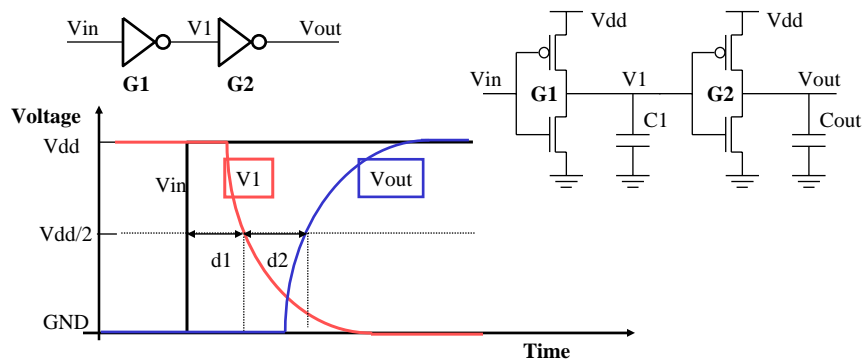

- Total Propagation Delay = Sum of individual delays = $d1 + d2$
- Capacitance $C1$ has two components:
 - Capacitance of the wire connecting the two gates
 - Input capacitance of the second inverter


UTCS

Slide courtesy of D. Patterson

Lecture 2

21

Review: Calculating Delays

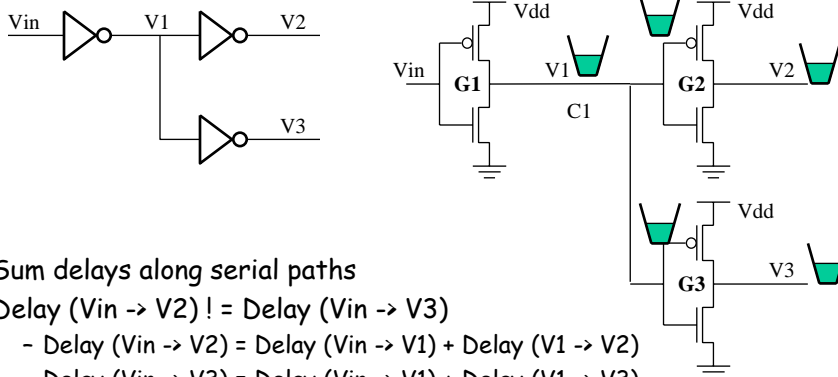

- Sum delays along serial paths
- Delay ($V_{in} \rightarrow V2$) \neq Delay ($V_{in} \rightarrow V3$)
 - Delay ($V_{in} \rightarrow V2$) = Delay ($V_{in} \rightarrow V1$) + Delay ($V1 \rightarrow V2$)
 - Delay ($V_{in} \rightarrow V3$) = Delay ($V_{in} \rightarrow V1$) + Delay ($V1 \rightarrow V3$)
- Critical Path = The longest among the N parallel paths
- $C1 = \text{Wire } C + C_{in} \text{ of Gate } 2 + C_{in} \text{ of Gate } 3$

UTCS


Slide courtesy of D. Patterson

Lecture 2


22

Clocking and Clocked Elements

 - Typical Clock
 - 1Hz = 1 cycle per second




- Transparent Latch

 

CLK=0, Q=oldQ
CLK=1, Q=D

- Edge Triggered Flip-Flop

 


UTCS

Lecture 2

23

Storage Element's Timing Model

 

- Setup Time: Input must be stable BEFORE the trigger clock edge
- Hold Time: Input must REMAIN stable after the trigger clock edge
- Clock-to-Q time:
 - Output cannot change instantaneously at the trigger clock edge
 - Similar to delay in logic gates, two components:
 - Internal Clock-to-Q
 - Load dependent Clock-to-Q


UTCS

Slide courtesy of D. Patterson

Lecture 2


24

Clocking Methodology

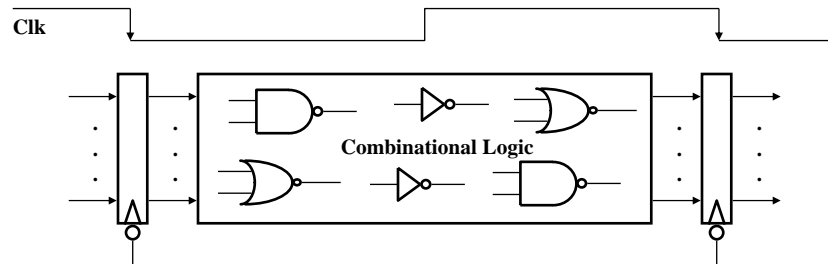

- All storage elements are clocked by the same clock edge
- The combination logic block's:
 - Inputs are updated at each clock tick
 - All outputs **MUST** be stable before the next clock tick



Critical Path & Cycle Time

 


- Critical path: the slowest path between any two storage devices
- Cycle time is a function of the critical path
- must be greater than:
 - Clock-to-Q + Longest Path through the Combination Logic + Setup

Tricks to Reduce Cycle Time

- Reduce the number of gate levels

  

 - Pay attention to loading
 - One gate driving many gates is a bad idea
 - Avoid using a small gate to drive a long wire
- Use multiple stages to drive large load




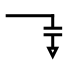

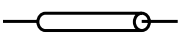

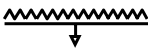
UTCS

Slide courtesy of D. Patterson

Lecture 2

27

Wires

- Limiting Factor
 - Density
 - Speed
 - Power
- 3 models for wires (model to use depends on switching frequency)
 - Short  
 - Lossless  
 - Lossy  


UTCS

Lecture 2

28

Wire Density

 - Communication constraints
 - Must be able to move bits to/from storage and computation elements
- Example: 9 ported register file




UTCS

Lecture 2

29

Chip Level

 

UTCS

Lecture 2

30

Board Level



Stanford Imagine Board

UTCS

Lecture 2

31

Rack Level



MIT J-Machine

UTCS




DOE ASCI White

Lecture 2

32

Memory

 - Moves information in time (wires move it in space)
- Provides state
- Requires energy to change state
 - Feedback circuit - SRAM
 - Capacitors - DRAM
 - Magnetic media - disk
- Required for memories
 - Storage medium
 - Write mechanism
 - Read mechanism



4Gb DRAM Die

Technology Scaling Trends

- CPU Transistor density - 60% per year
- CPU Transistor speed - 15% per year
- DRAM density - 60% per year
- DRAM speed - 3% per year
- On-chip wire speed - decreasing relative to transistors (witness the Pentium 4 pipeline)
- Off-chip pin bandwidth - increasing, but slowly
- Power - approaching costs limits
 - $P = CV^2f + I_{leak}V$
- All of these factors affect the end system architecture


Summary

- Logic Transistors + Wires + Storage = Computer!
- Transistors
 - Composable switches
 - Electrical considerations
 - Delay from parasitic capacitors and resistors
 - Power ($P = CV^2f$)
- Wires
 - Becoming more important from delay and BW perspective
- Memories
 - Density, Access time, Persistence, BW

Performance Measurement and Evaluation

Many Dimensions to Performance

 - CPU execution time
 - by instruction or sequence
 - floating point
 - integer
 - branch performance
- Cache bandwidth
- Main memory bandwidth
- I/O performance
 - bandwidth
 - seeks
 - pixels or polygons per second
- Relative importance depends on applications



Evaluation Tools

- Benchmarks, traces, & mixes


- macrobenchmarks & suites
 - application execution time
- microbenchmarks
 - measure one aspect of performance
- traces
 - replay recorded accesses
 - cache, branch, register

MOVE	39%
BR	20%
LOAD	20%
STORE	10%
ALU	11%

```
LD 5EA3
ST 31FF
....
LD 1EA2
....
```

- Simulation at many levels

 - ISA, cycle accurate, RTL, gate, circuit
 - trade fidelity for simulation rate



- Area and delay estimation

- Analysis

- e.g., queuing theory

Next Time

- Evaluation of Systems

- Performance
 - Amdahl's Law, CPI
- Cost
- Benchmark Examples

- Reading assignment

- P&H Chapter 4 - Performance measurement