 


Lecture 8: Datapaths and Pipelining

- Last Time
 - Last of the ISA lectures
- Today
 - Role of compiler
 - Datapath organization
 - Datapath control

Instruction Execution

- 5 basic steps
 - fetch instruction (F)
 - decode instruction and read registers (R)
 - execute (X)
 - access memory (M)
 - store result (W)







The Processor: Datapath & Control

- We're ready to look at an implementation of the MIPS
- Simplified to contain only:
 - memory-reference instructions: `lw, sw`
 - arithmetic-logical instructions: `add, sub, and, or, slt`
 - control flow instructions: `beq, j`
- Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
- All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?

©2004 Morgan Kaufmann Publishers 3


Pieces we'll need

    

©2004 Morgan Kaufmann Publishers 4

More Implementation Details

- **Abstract / Simplified View:**


 


Two types of functional units:

- elements that operate on data values (combinational)
- elements that contain state (sequential)

Register File


- **Built using D flip-flops**

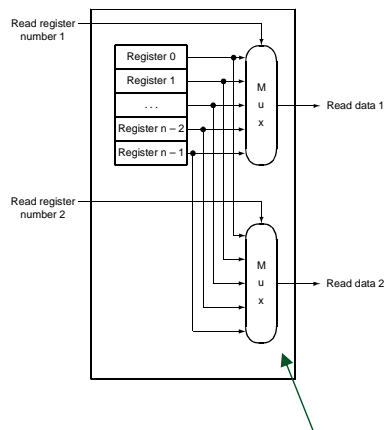 

Do you understand? What is the "Mux" above?

Abstraction

 
- Make sure you understand the abstractions!
- Sometimes it is easy to think you do, when you don't



©2004 Morgan Kaufmann Publishers 7

Register File

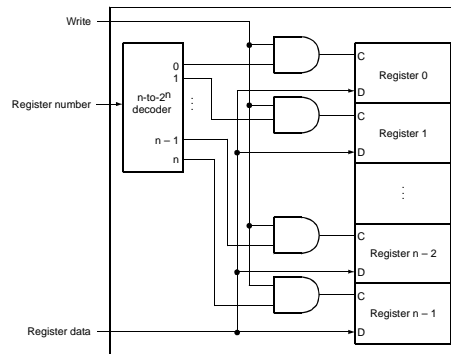
- Note: we still use the real clock to determine when to write



©2004 Morgan Kaufmann Publishers 8


Simple Implementation

 - Include the functional units we need for each instruction




Why do we need this stuff?


ADD Instruction – instruction fetch

 

ADD Instruction – the whole thing

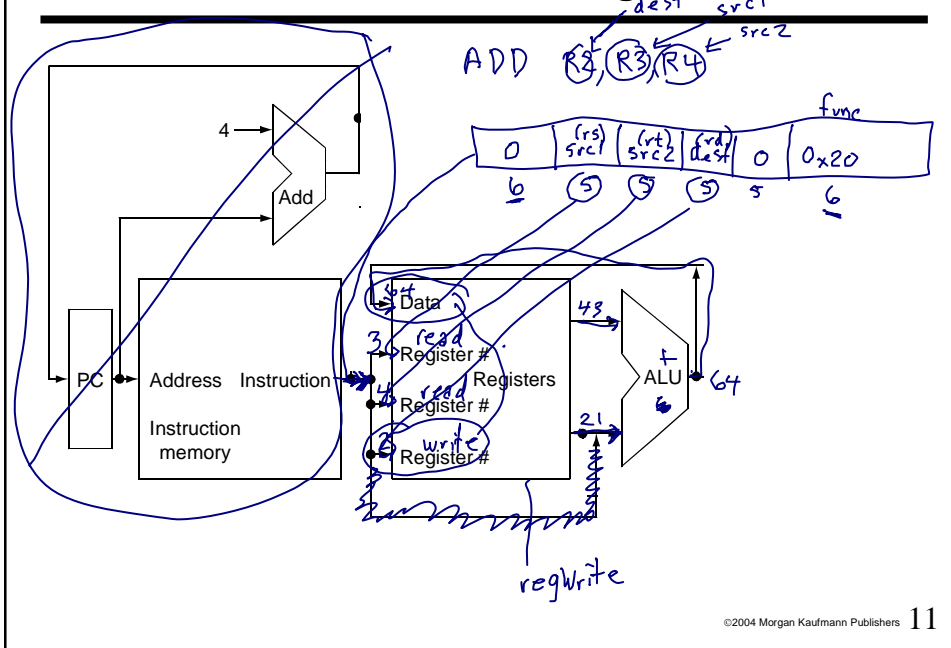


LW/SW Instruction

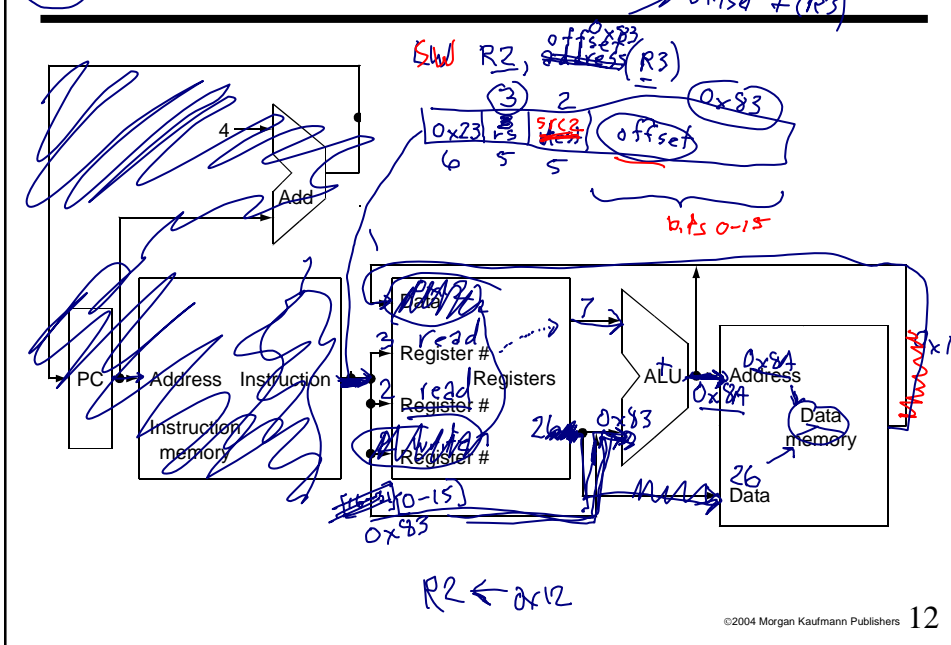

BEQ Instruction


BEQ R2, R3, offset

← address in assembler!

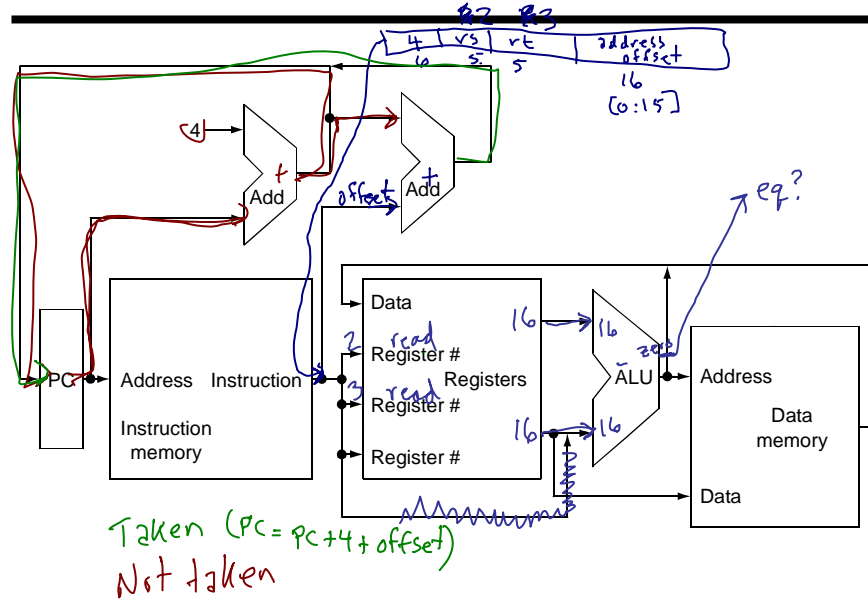

Building the Datapath

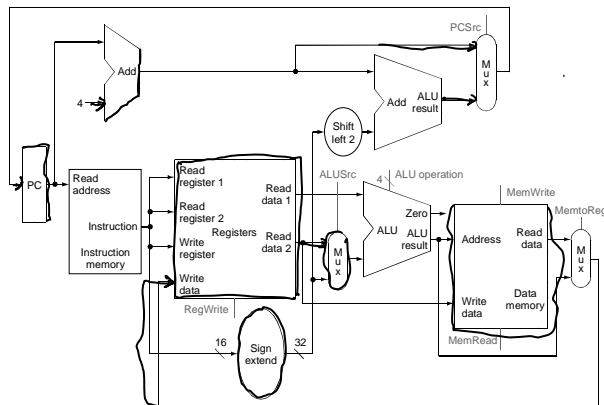- Use multiplexers to stitch them together



Control

- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:

add \$8, \$17, \$18

Instruction Format:

000000	10001	10010	01000	00000	100000
op	rs	rt	rd	shamt	funct

- ALU's operation based on instruction type and function code